
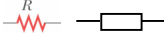







Physics 202, Lecture 10

Today's Topics

- DC Circuits (2)
 - Kirchhoff's Rules
 - RC Circuits
- Announcements:
 - Homework #4 due Monday, 10/8 at 10 PM
 - Reading quiz (optional): open until Friday, 10/5 5 PM


Basic Circuit Components

| Component | Symbol | Behavior in circuit |
|-------------------------|---|--|
| Ideal battery, emf |  | $\Delta V = V_+ - V_- = \mathcal{E}$ |
| Resistor |  | $\Delta V = -IR$ |
| Realistic Battery |  | $\rightarrow \begin{matrix} \mathcal{E} \\ \text{---} \text{---} r \end{matrix}$ |
| (Ideal) wire |  | $\Delta V = 0 \quad (\rightarrow R=0, C=0)$ |
| Capacitor |  | $\Delta V = V_- - V_+ = -q/C, dq/dt = I$ |
| Inductor |  | later in semester |
| (Ideal) Switch |  | $C=0, R=0 \text{ (on)}, R=\infty \text{ (off)}$ |
| Transformer | Future Topics | |
| Diodes, Transistors,... | | |

Circuit Analysis

**General circuits:
more complicated topology**

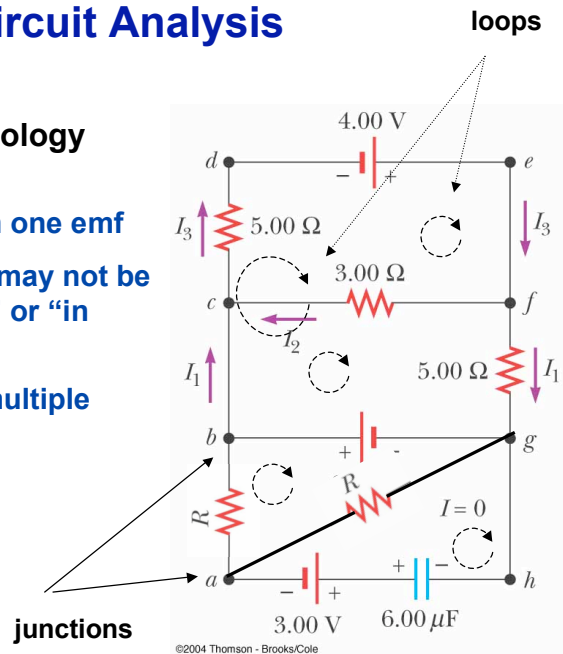- may contain more than one emf
- resistor combinations may not be as simple as “in series” or “in parallel”
- Circuits may contain multiple loops and junctions.



Circuit Analysis

Kirchoff's Laws

#1 Conservation of electric charge

All the charge that flows into a junction of conductors per unit time, the same amount must leave in the same time interval.

#2 Conservation of energy


A complete trip around the circuit (the end point is the same as the beginning point) must result in zero net energy change.

Kirchhoff's Rules: Junction Rule

□ Rule #1: Junction Rule

The net current entering **any** junction equals the net current leaving that junction.
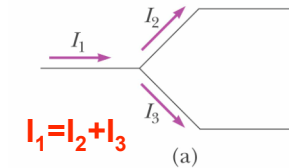
$$\Sigma I_{\text{in}} = \Sigma I_{\text{out}}$$



□ Determined by **assigned direction** for each current:

- “in” : current with **assigned direction** towards junction
- “out” : current with **assigned direction** off junction


(Very) Quick Quiz: Junction Rule

□ What is the junction rule for the current assignment shown?

$$I_1 + I_2 = I_3$$

$$I_1 = I_2 + I_3$$

$$I_1 - I_2 = I_3$$

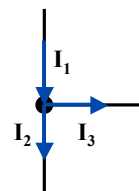

Although equation 2 and 3 are equivalent, equation 3 does not follow template form $I_{\text{in}} = I_{\text{out}}$


Quick Quiz: Junction Rule

- ❑ What is the junction rule for the current assignment shown?

$$I_1 + I_2 = I_3$$

$$I_1 + I_2 + I_3 = 0$$

Neither

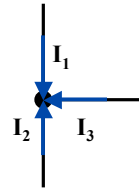


While the actual currents can not all go into a junction, the assigned currents can.

Kirchhoff's Rules: Loop Rule

- ❑ Loop Rule (Energy Conservation):

The sum of **potential drops** across components along **any closed** circuit loop must be zero.



$$\sum \Delta V = 0$$

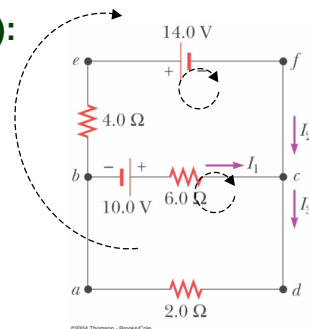

- The exact expression of the potential drop is determined by the type of component **and the assigned current direction** (see next slides)

Determine Potential Difference(1)

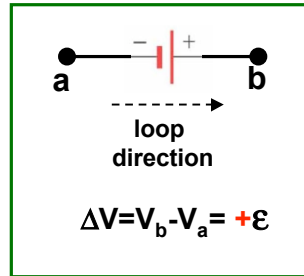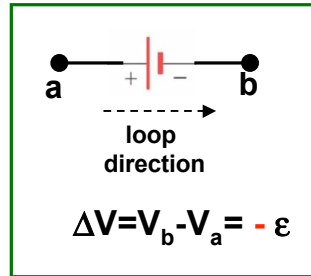Choose a direction for the current, and move around the loop in that direction.





When a battery is traversed from the positive terminal to the negative terminal, the voltage drops (- sign).

When a battery is traversed from the negative terminal to the positive terminal, the voltage increases (+ sign).

Determine Potential Differences (2)

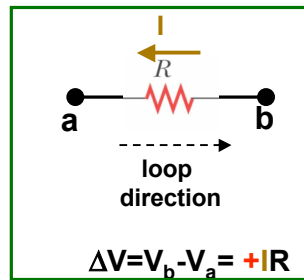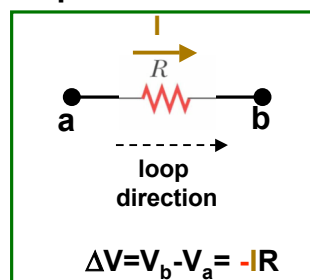Choose a direction for the current, and move around the loop in that direction.





When moving across a resistor in the direction of the assigned current, the voltage drops (- sign).

When moving across a resistor in a direction opposite to the assigned current, the voltage increases (+ sign).

Determine Potential Differences (3)

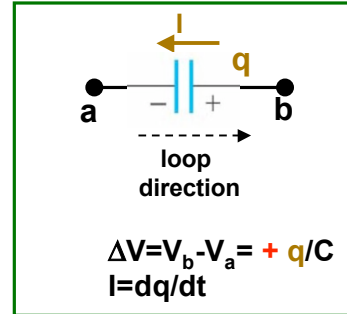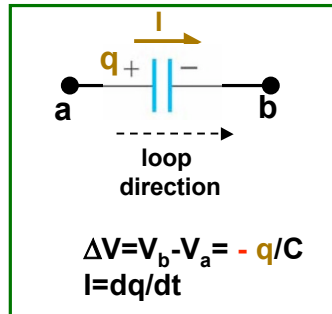Choose a direction for the current, and move around the loop in that direction.



When moving across a capacitor from the positive plate to the negative plate, the voltage drops (- sign).

When moving across a capacitor from the negative plate to the positive plate, the voltage increases (+ sign).

Steps to Apply Kirchhoff's Rules

1. Assign directional currents for each branch of the circuit.
2. Set up junction rules at certain (any) junctions. Normally, # of junctions = # of currents - 1.
3. Select a number of closed loops to apply loop rule.
For each, follow a clockwise (or counterclockwise) direction, find ΔV across each component, apply loop rule.
of loops determined by # of unknowns.
4. Solve for unknowns. (A negative current indicates its direction is opposite to the assigned direction.)

Example 1: Resistors In Series


□ Show $R_{eq} = R_1 + R_2$.

Applying Kirchhoff Rules:

Junction a: $I_1 = I$

Junction c: $I_2 = I$

Loop: $\Delta V - I_1 R_1 - I_2 R_2 = 0$

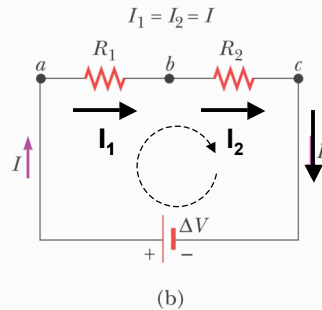

©2004 Thomson - Brooks/Cole

□ Questions:

- What are the voltage drops across R_1 and R_2 ?
- What is the power delivered to R_1 and R_2 ?

Example 2: Resistors In Parallel


□ Show $1/R_{eq} = 1/R_1 + 1/R_2$.

Applying Kirchhoff Rules:

Junction: $I_1 + I_2 = I$

Loop 1: $\Delta V - I_1 R_1 = 0$

Loop 2: $\Delta V - I_2 R_2 = 0$

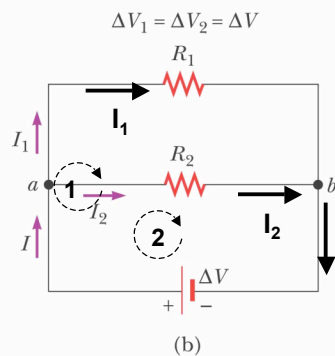

©2004 Thomson - Brooks/Cole

□ Questions:

- What are the voltage drops across R_1 and R_2 ?
- What is the power delivered to R_1 and R_2 ?

Multi-loop examples

- ❑ On board: two loop circuit example
Ch. 28 # 21 (28 if time)
- ❑ On board: three loop circuit example
Ch. 28, #26 (25 if time)
- ❑ On slides: textbook example 28.9

Example 3: Multi-Loop

- ❑ (Text example 28.9)

Find out I_1 , I_2 , I_3

- ❑ Kirchhoff's Rules:

Junction c:

$$I_1 + I_2 = I_3$$

Loop 1:

$$\mathcal{E}_1 - I_1 R_1 - I_3 R_3 = 0$$


Loop 2:

$$-\mathcal{E}_2 + I_1 R_1 - \mathcal{E}_1 - I_2 R_2 = 0$$


Solving three equations:

$$I_1 = 2.0\text{A}, I_2 = -3.0\text{A}, I_3 = -1.0\text{A},$$

What does the $-$ sign mean?

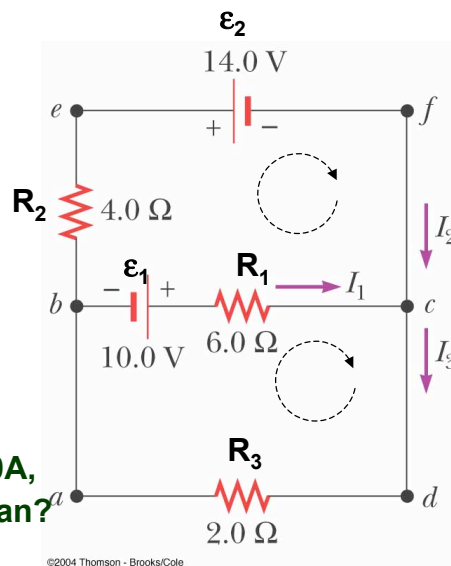

Example 3: Interpretation of Results

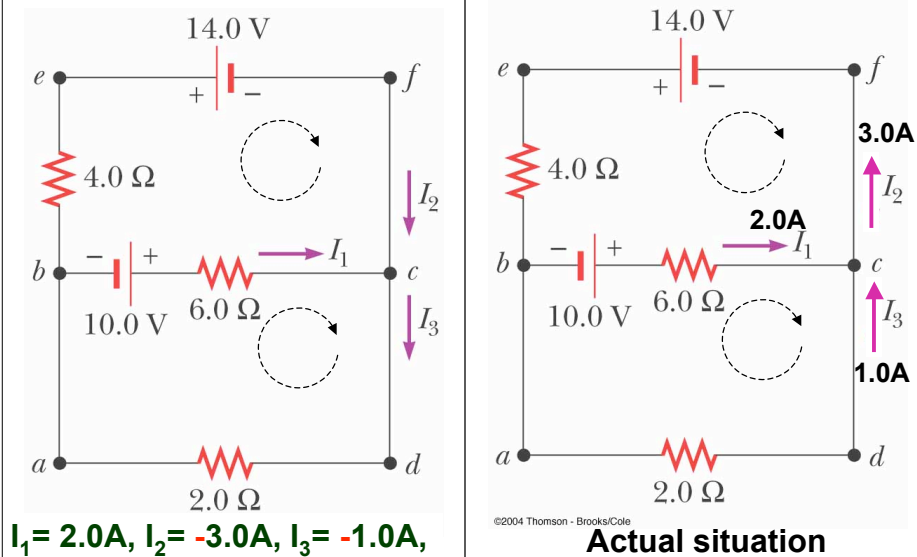

Example 3 Again: Different Initial Directions

Different initial direction for I_1, I_2

□ Apply Kirchhoff's Rules:

Junction c:

$$0 = I_3 + I_1 + I_2$$

Loop 1:

$$\mathcal{E}_1 + I_1 R_1 - I_3 R_3 = 0$$


Loop 2:

$$-\mathcal{E}_2 - I_1 R_1 - \mathcal{E}_1 + I_2 R_2 = 0$$

Solving three equations:


$$I_1 = -2.0\text{A}, I_2 = +3.0\text{A}, I_3 = -1.0\text{A},$$

Same result as previous slide

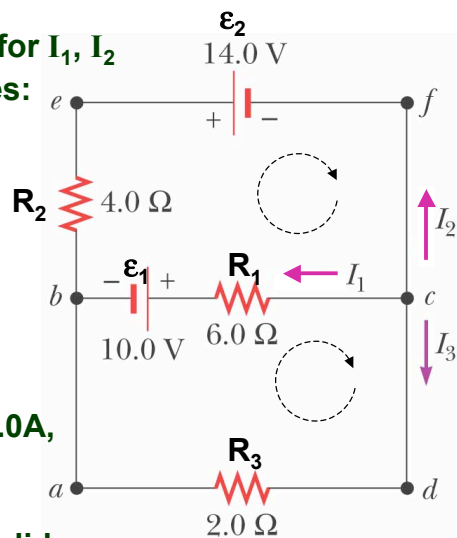


RC Circuits

First example: time-dependent currents

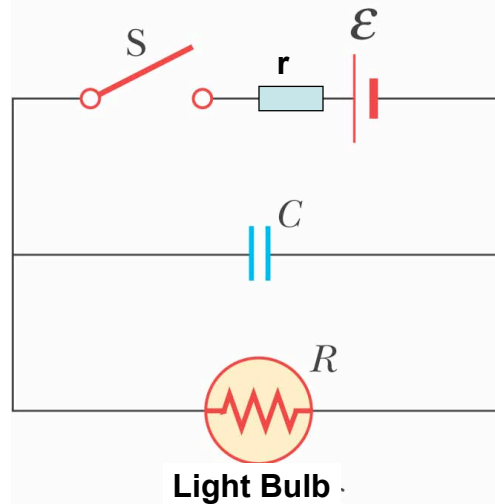


Charging A Capacitor in RC Circuit

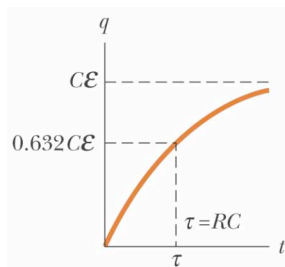- Find I and q when a capacitor is being charged in a RC circuit (see board).




$$q(t) = \mathcal{E}C(1 - e^{-t/RC})$$

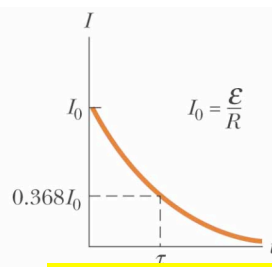

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

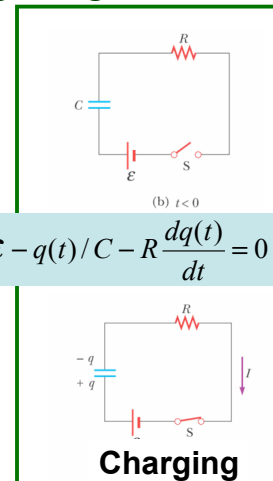Note: $\tau \equiv RC$ is the “time constant”



Discharging A Capacitor in RC Circuit

- Find I , q when a capacitor is being discharged in a RC circuit (See board).

$$q(t) = Qe^{-t/RC}$$

$$I(t) = -\frac{Q}{RC}e^{-t/RC}$$

Note the time constant $\tau = RC$

