

Physics 202
Chapter 32 continued
Oct 30, 2007




Induction:
LC circuit, RLC circuit

On whiteboard

- LC circuit
 - Solve Kirchhoff's equation
 - Harmonic oscillator
 - Discussion
 - analogy to mass spring system
 - Energy
- RLC circuit
 - Solution
 - Demonstration with a weakly damped RLC circuit

LC Circuits

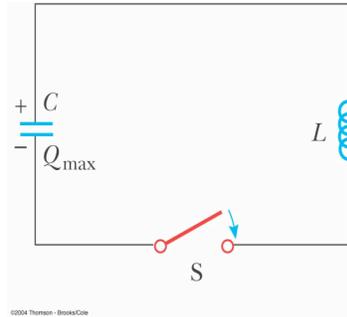- Assume the capacitor is initially charged and then the switch is closed
- Assume no resistance and no energy losses to radiation
- The current in the circuit and the charge on the capacitor oscillate between maximum positive and negative values
- With zero resistance, no energy is dissipated.



- Kirchoff's loop rule:

$$-\frac{Q}{C} - L \frac{dI}{dt} = 0$$

Discussion on whiteboard....

Derivation of LC and RLC circuit.


LC oscillator

- Initially energy stored in the electric field in the capacitor



$$U = \frac{Q^2}{2C}$$
- Then energy transferred to B-field

$$U = \frac{1}{2} L \cdot I^2$$
- And so forth ...

LC oscillator

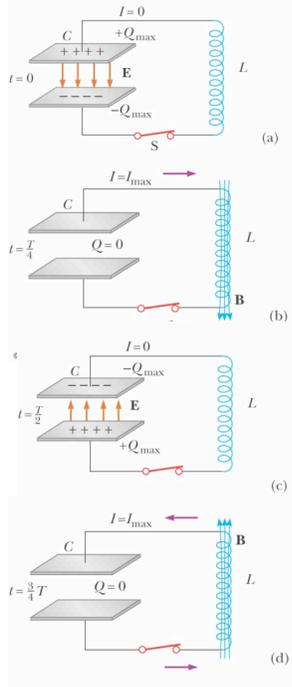

Time [T]	Q [Q _{Max}]	I [I _{Max}]
0	1	0
1/4	0	1
1/2	-1	0
3/4	0	-1
1	1	0

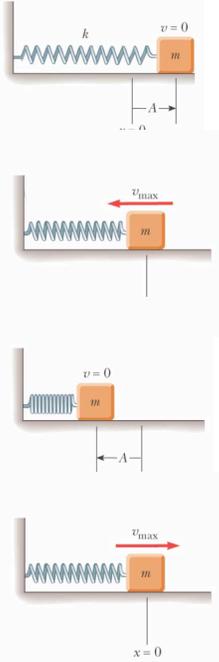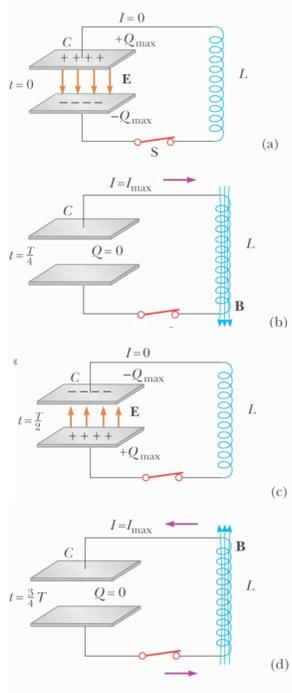

Analogy to mechanical harmonic oscillator

Oscillations in an LC Circuit

- The energy continues to oscillate between the inductor and the capacitor
- The total energy stored in the LC circuit remains constant in time and equals

$$U = U_C + U_L = \frac{Q^2}{2C} + \frac{1}{2}LI^2$$

Time Functions of an LC Circuit

- In an LC circuit, charge can be expressed as a function of time
 - $Q = Q_{\max} \cos(\omega t + \varphi)$
 - This is for an ideal LC circuit
- The angular frequency, ω , of the circuit depends on the inductance and the capacitance
 - It is the *natural frequency* of oscillation of the circuit

$$\omega = \frac{1}{\sqrt{LC}}$$

Time Functions of an LC Circuit, 2

- The charge can be expressed as a function of time



$$Q = Q_{\max} \cos(\omega t + \varphi)$$

- The current:


$$I = \frac{dQ}{dt} = -\omega Q_{\max} \sin(\omega t + \varphi)$$

- The total energy
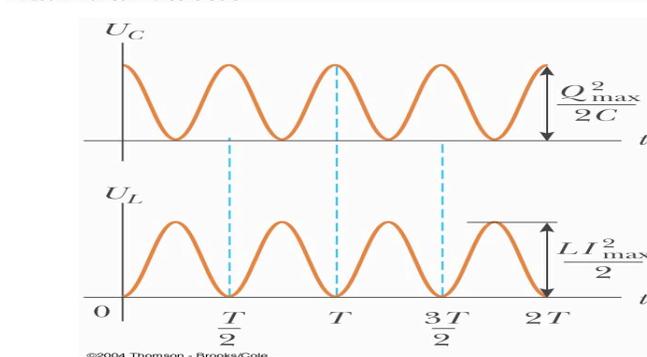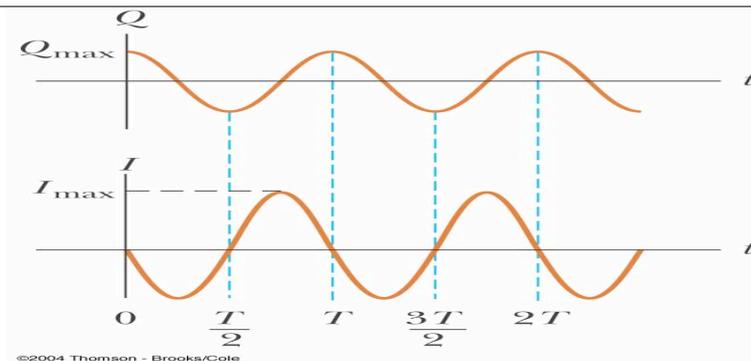
$$U = U_C + U_L = \frac{Q_{\max}^2}{2C} \cos^2 \omega t + \frac{1}{2} L I_{\max}^2 \sin^2 \omega t$$



The *RLC* Circuit

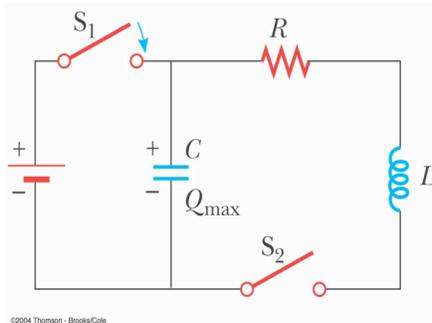

Kirchoff's rule gives:

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

RLC Circuit - a damped harmonic oscillator

- When R is small:
 - The *RLC* circuit is analogous to light damping in a mechanical oscillator
 - $Q = Q_{\max} e^{-Rt/2L} \cos \omega_d t$
 - ω_d is the angular frequency of oscillation for the circuit and

$$\omega_d = \left[\frac{1}{LC} - \left(\frac{R}{2L} \right)^2 \right]^{1/2}$$

RLC Circuit - Damped Oscillator

- When R is very large, the oscillations damp out very rapidly
- There is a critical value of R above which no oscillations occur
- If $R = R_c$, the circuit is said to be *critically damped*
- When $R > R_c$, the circuit is said to be *overdamped*

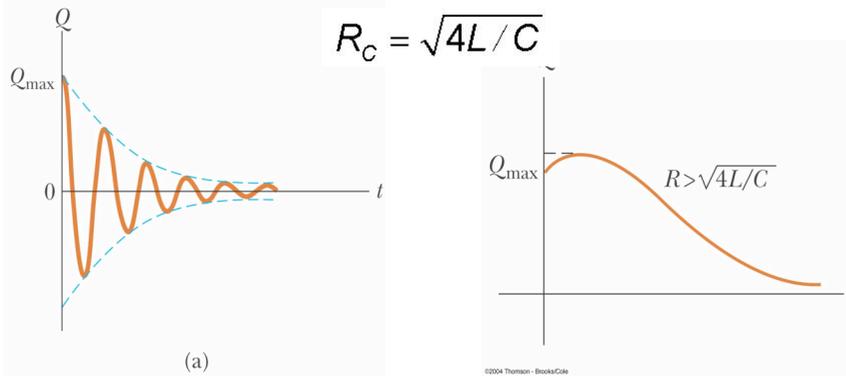


Table 32.1

Analogies Between Electrical and Mechanical Systems

Electric Circuit		One-Dimensional Mechanical System
Charge	$Q \leftrightarrow x$	Position
Current	$I \leftrightarrow v_x$	Velocity
Potential difference	$\Delta V \leftrightarrow F_x$	Force
Resistance	$R \leftrightarrow b$	Viscous damping coefficient
Capacitance	$C \leftrightarrow 1/k$	($k =$ spring constant)
Inductance	$L \leftrightarrow m$	Mass
Current = time derivative of charge	$I = \frac{dQ}{dt} \leftrightarrow v_x = \frac{dx}{dt}$	Velocity = time derivative of position
Rate of change of current = second time derivative of charge	$\frac{dI}{dt} = \frac{d^2Q}{dt^2} \leftrightarrow a_x = \frac{dv_x}{dt} = \frac{d^2x}{dt^2}$	Acceleration = second time derivative of position
Energy in inductor	$U_L = \frac{1}{2} LI^2 \leftrightarrow K = \frac{1}{2} mv^2$	Kinetic energy of moving object
Energy in capacitor	$U_C = \frac{1}{2} \frac{Q^2}{C} \leftrightarrow U = \frac{1}{2} kx^2$	Potential energy stored in a spring
Rate of energy loss due to resistance	$I^2R \leftrightarrow bv^2$	Rate of energy loss due to friction
RLC circuit	$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \leftrightarrow m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0$	Damped object on a spring

© 2004 Thomson - Brooks/Cole