

Homework 8:

Problem 1:

P32.52 (a) $f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.100 \text{ H})(1.00 \times 10^{-6} \text{ F})}} = \boxed{503 \text{ Hz}}$

(b) $Q = C\varepsilon = (1.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = \boxed{12.0 \mu\text{C}}$

(c) $\frac{1}{2}C\varepsilon^2 = \frac{1}{2}LI_{\text{max}}^2$
 $I_{\text{max}} = \varepsilon\sqrt{\frac{C}{L}} = 12 \text{ V}\sqrt{\frac{1.00 \times 10^{-6} \text{ F}}{0.100 \text{ H}}} = \boxed{37.9 \text{ mA}}$

(d) At all times $U = \frac{1}{2}C\varepsilon^2 = \frac{1}{2}(1.00 \times 10^{-6} \text{ F})(12.0 \text{ V})^2 = \boxed{72.0 \mu\text{J}}$.

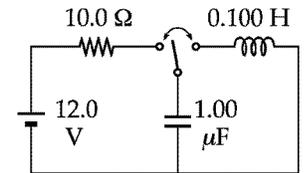


FIG. P32.52

Problem 2:

P57: The period of damped oscillation is $T = \frac{2\pi}{\omega_d}$. After one oscillation the charge returning to the capacitor is $Q = Q_{\text{max}}e^{-RT/2L} = Q_{\text{max}}e^{-2\pi R/2L\omega_d}$. The energy is proportional to the charge squared, so after one oscillation it is $U = U_0e^{-2\pi R/L\omega_d} = 0.99U_0$. Then

$$e^{2\pi R/L\omega_d} = \frac{1}{0.99}$$

$$\frac{2\pi R}{L\omega_d} = \ln(1.0101) = 0.001005$$

$$L\omega_d = \frac{2\pi R}{0.001005} = 1250 \Omega = L\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)^{1/2}$$

$$1.563 \times 10^6 \Omega^2 = \frac{L}{C} - \frac{(2 \Omega)^2}{4}$$

$$\frac{L}{C} = 1.563 \times 10^6 \Omega^2$$

We are also given

$$\omega = 2\pi \times 10^3 / \text{s} = \frac{1}{\sqrt{LC}}$$

$$LC = \frac{1}{(2\pi \times 10^3 / \text{s})^2} = 2.533 \times 10^{-8} \text{ s}^2$$

Solving simultaneously,

$$C = 2.533 \times 10^{-8} \text{ s}^2 / L$$

$$\frac{L^2}{2.533 \times 10^{-8} \text{ s}^2} = 1.563 \times 10^6 \Omega^2 \quad \boxed{L = 0.199 \text{ H}}$$

$$C = \frac{2.533 \times 10^{-8} \text{ s}^2}{0.199 \text{ H}} = \boxed{127 \text{ nF} = C}$$

PROBLEM 3:

$$i_L(t) = \frac{\Delta V_{\max}}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right) = \frac{(80.0 \text{ V}) \sin\left[(65.0\pi)(0.0155) - \pi/2\right]}{(65.0\pi \text{ rad/s})(70.0 \times 10^{-3} \text{ H})}$$

$$i_L(t) = (5.60 \text{ A}) \sin(1.59 \text{ rad}) = \boxed{5.60 \text{ A}}$$

PROBLEM 4:

P33.33 (a) $P = I_{\text{rms}}(\Delta V_{\text{rms}}) \cos \phi = (9.00)180 \cos(-37.0^\circ) = 1.29 \times 10^3 \text{ W}$
 $P = I_{\text{rms}}^2 R$ so $1.29 \times 10^3 = (9.00)^2 R$ and
 $R = \boxed{16.0 \Omega}$.

(b) $\tan \phi = \frac{X_L - X_C}{R}$ becomes $\tan(-37.0^\circ) = \frac{X_L - X_C}{16}$: so
 $X_L - X_C = \boxed{-12.0 \Omega}$.

PROBLEM 5:

(a) $f = \frac{1}{2\pi\sqrt{LC}}$

$$C = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4\pi^2 (10^{10}/\text{s})^2 400 \times 10^{-12} \text{ Vs}} \left(\frac{\text{C}}{\text{As}}\right) = \boxed{6.33 \times 10^{-13} \text{ F}}$$

(b) $C = \frac{\kappa \epsilon_0 A}{d} = \frac{\kappa \epsilon_0 \ell^2}{d}$

$$\ell = \left(\frac{Cd}{\kappa \epsilon_0}\right)^{1/2} = \left(\frac{6.33 \times 10^{-13} \text{ F} \times 10^{-3} \text{ mm}}{1 \times 8.85 \times 10^{-12} \text{ F}}\right)^{1/2} = \boxed{8.46 \times 10^{-3} \text{ m}}$$

(c) $X_L = 2\pi fL = 2\pi \times 10^{10}/\text{s} \times 400 \times 10^{-12} \text{ Vs/A} = \boxed{25.1 \Omega}$

PROBLEM 6:

P33.46 (a) $(\Delta V_{2, \text{rms}}) = \frac{N_2}{N_1} (\Delta V_{1, \text{rms}})$ $N_2 = \frac{(2200)(80)}{110} = \boxed{1600 \text{ windings}}$

(b) $I_{1, \text{rms}} (\Delta V_{1, \text{rms}}) = I_{2, \text{rms}} (\Delta V_{2, \text{rms}})$ $I_{1, \text{rms}} = \frac{(1.50)(2200)}{110} = \boxed{30.0 \text{ A}}$

(c) $0.950 I_{1, \text{rms}} (\Delta V_{1, \text{rms}}) = I_{2, \text{rms}} (\Delta V_{2, \text{rms}})$ $I_{1, \text{rms}} = \frac{(1.20)(2200)}{110(0.950)} = \boxed{25.3 \text{ A}}$

PROBLEM 7:

$$(a) \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{68.0^2 + (16.0 - 101)^2} = \boxed{109 \Omega}$$

$$X_L = \omega L = (100)(0.160) = 16.0 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(100)(99.0 \times 10^{-6})} = 101 \Omega$$

$$(b) \quad I_{\max} = \frac{\Delta V_{\max}}{Z} = \frac{40.0 \text{ V}}{109 \Omega} = \boxed{0.367 \text{ A}}$$

$$(c) \quad \tan \phi = \frac{X_L - X_C}{R} = \frac{16.0 - 101}{68.0} = -1.25 :$$

$$\phi = -0.896 \text{ rad} = -51.3^\circ$$

$$\boxed{I_{\max} = 0.367 \text{ A}} \quad \boxed{\omega = 100 \text{ rad/s}} \quad \boxed{\phi = -0.896 \text{ rad} = -51.3^\circ}$$

PROBLEM 8:

P33.53 For this RC high-pass filter, $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{R}{\sqrt{R^2 + X_C^2}}$.

$$(a) \quad \text{When } \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = 0.500,$$

$$\text{then } \frac{0.500 \Omega}{\sqrt{(0.500 \Omega)^2 + X_C^2}} = 0.500 \text{ or } X_C = 0.866 \Omega.$$

If this occurs at $f = 300 \text{ Hz}$, the capacitance is

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(300 \text{ Hz})(0.866 \Omega)} = 6.13 \times 10^{-4} \text{ F} = \boxed{613 \mu\text{F}}.$$

$$(b) \quad \text{With this capacitance and a frequency of } 600 \text{ Hz},$$

$$X_C = \frac{1}{2\pi(600 \text{ Hz})(6.13 \times 10^{-4} \text{ F})} = 0.433 \Omega$$

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{0.500 \Omega}{\sqrt{(0.500 \Omega)^2 + (0.433 \Omega)^2}} = \boxed{0.756}.$$

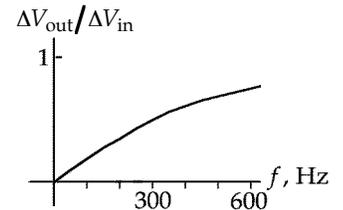
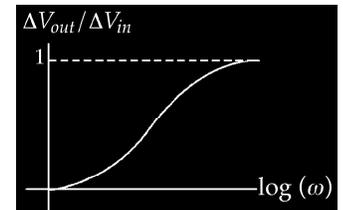
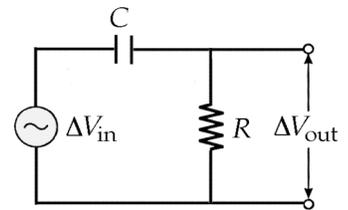


FIG. P33.53

PROBLEM 9:

P33.35 Consider a two-wire transmission line:

$$I_{\text{rms}} = \frac{P}{\Delta V_{\text{rms}}} \quad \text{and power loss} = I_{\text{rms}}^2 R_{\text{line}} = \frac{P}{100}.$$

$$\text{Thus, } \left(\frac{P}{\Delta V_{\text{rms}}} \right)^2 (2R_1) = \frac{P}{100} \quad \text{or}$$

$$R_1 = \frac{(\Delta V_{\text{rms}})^2}{200P}$$

$$R_1 = \frac{\rho d}{A} = \frac{(\Delta V_{\text{rms}})^2}{200P} \quad \text{or}$$

$$A = \frac{\pi(2r)^2}{4} = \frac{200\rho P d}{(\Delta V_{\text{rms}})^2}$$

and the diameter is

$$2r = \sqrt{\frac{800\rho P d}{\pi(\Delta V)^2}}.$$

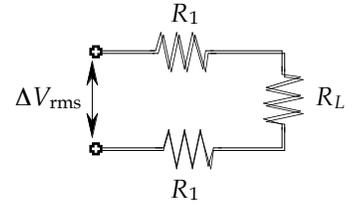


FIG. P33.35